Cairo University Faculty of Engineering

Credit Hours System



Computer Architecture CMPN301

Computer Architecture Project Phase 1 Report

Team Members:

Ahmed Magdy Abdelaziz 1190200

Mahmoud Khaled Mahmoud 1190141

Ziad Ezzat Sedky 1190032

Ahmed Mohamed Saad Hussein 1190184

Instructions Sequence:

Instructions divided into 4 categories:

- Instructions with no operand
- Instructions with only one operands
- Instructions with only two operands
- Instructions with three operands
- 1) Instructions with no operand:

Divided into 3 groups as following:

- CLRC, SETC → For carry bit
- RET , RTI → For Memory (SP to PC)
- NOP
- 2) Instructions with one operand:

Divided into 2 Groups as following:

- 1) Read from register file and this divided into 4 Groups:
 - OUT → Destination is OUT port
 - PUSH → Destination is Memory
 - JMP , JZ , JC → Destination is PC
 - CALL → Destination is PC and Memory
- 2) Write into register file and this divided into 2 Groups:
 - 1) IN \rightarrow Source is IN Port
 - 2) POP → Source is Memory
- 3) Instructions with two operands:

Divided into 4 groups as following:

- 1) Memory:
 - LOAD
 - 1. LDM \rightarrow SRC will be immediate value
 - 2. LDD \rightarrow SRC will be any Register

- Store → STD
- 2) MOV
- 3) NOT
- 4) INC or DEC
- 4) Instructions with Three operands:

Divided into 4 Groups as following:

- 1) Adding:
 - ADD → SRC2 will be from Register file
 - IADD → will read from Immediate value
- 2) SUB
- 3) AND
- 4) OR

Instruction details:

Total Instruction → 32 bits

RDST & RSRC1 & RSRC2 \rightarrow 3-bits , X \rightarrow Don't Care , IMM (16 bits immediate value)

NOTE) Colored bits means \rightarrow will be read from Register File

- 1) NOP \rightarrow 00 RDST RSRC1 RSRC2 X 00 XX IMM
- 2) SETC → 00 RDST RSRC1 RSRC2 0 01 XX IMM
- 3) CLRC \rightarrow 00 RDST RSRC1 RSRC2 1 01 XX IMM
- 4) RET \rightarrow 00 RDST RSRC1 RSRC2 0 10 XX IMM
- 5) RTI \rightarrow 00 RDST RSRC1 RSRC2 1 10 XX IMM
 - [31:30] \rightarrow Identify one of four categories that mentioned above
 - [19:18] → Select one operation from the selected category

```
31:30 rd:rs1:rs2 20: 19:18 17:16
```

- 6) OUT \rightarrow 01 RDST RSRC1 RSRC2 0 00 XX IMM
- 7) PUSH \rightarrow 01 RDST RSRC1 RSRC2 0 01 XX IMM
- 8) JZ \rightarrow 01 RDST RSRC1 RSRC2 0 10 10 IMM
- 9) JC \rightarrow 01 RDST RSRC1 RSRC2 0 10 01 IMM
- 10) JMP \rightarrow 01 RDST RSRC1 RSRC2 0 10 11 IMM
- 11) CALL \rightarrow 01 RDST RSRC1 RSRC2 0 11 11 IMM
- 12) IN \rightarrow 01 RDST RSRC1 RSRC2 1 00 XX IMM
- 13) POP \rightarrow 01 RDST RSRC1 RSRC2 1 01 XX IMM
 - [31:30] → Select one of Categories mentioned above
 - [20] → Indicate Write operation or Read operation
 - [19:18] → Select one Operation from this Category
 - [17:16] > Not be used for all except JMP to Select which JMP
 - NOTE: IN/OUT has same [19:18] Select between them by bit 20
- 14) MOV → 10 RDST RSRC1 RSRC2 X 00 0X IMM
 - 15) NOT \rightarrow 10 RDST RSRC1 RSRC2 X 01 0X IMM (ALU)
 - 16) INC \rightarrow 10 RDST RSRC1 RSRC2 0 10 0X IMM (ALU)
 - 17) DEC \rightarrow 10 RDST RSRC1 RSRC2 1 10 0X IMM (ALU)
 - 18) LDM \rightarrow 10 RDST RSRC1 RSRC2 0 11 1X IMM (ALU + Imm)

- 19) LDD \rightarrow 10 RDST RSRC1 RSRC2 0 11 0X IMM
- 20) STD \rightarrow 10 RDST RSRC1 RSRC2 1 11 0X IMM

[31:30] → Select one of four categories mentioned above

[19:18] → Select which operation from this category

Notes: INC/DEC have same [19:18] select Add or sub by bit 20 and

LDM/ LDD have same [19:18] we will select IMM or Reg by anding bit [17] with [31] if 1 → REG and else IMM value (16-bits), Store also has same [19:18] as LDM/LDD but we distinct it from LOAD operations by bit [20]

- 21) ADD \rightarrow 11 RDST RSRC1 RSRC2 X 00 0X IMM (ALU)
- 22) IADD → 11 RDST RSRC1 RSRC2 X 00 1X IMM (ALU + Imm)
- 23) SUB \rightarrow 11 RDST RSRC1 RSRC2 X 01 0X IMM (ALU)
- 24) AND \rightarrow 11 RDST RSRC1 RSRC2 X 10 0X IMM (ALU)
- 25) OR \rightarrow 11 RDST RSRC1 RSRC2 X 11 0X IMM (ALU)

 $[31:30] \rightarrow$ Select one of four categories mentioned above


[19:18] → Select one operations from this category

Notes: ADD/IADD have same [19:18] and we will difference between them by bit [17] anding with bit 31 and if 1 \rightarrow IMM value will be used , else \rightarrow REG will be used


INST	JMP FLAG	WB	Mem src	Sp inc	Sp dec	Mem W	Alu_src
NOP	0	0	0	0	0	0	0
SETC	0	0	0	0	0	0	0
CLRC	0	0	0	0	0	0	0
CALL	1	0	1	1	0	1	0
JZ	depends->ZF	0	0	0	0	0	0
JC	depends->CF	0	0	0	0	0	0
JMP	1	0	0	0	0	0	0
RET	0	0	1	1	0	0	0
RTI	0	0	1	1	0	0	0
POP	0	1	1	1	0	0	0
PUSH	0	0	1	0	1	0	0
IN	0	1	0	0	0	0	1
OUT	0	0	0	0	0	0	0
STD	0	0	0	0	0	1	0
IADD	0	1	0	0	0	0	1
LDM	0	1	0	0	0	0	0
LDD	0	1	0	0	0	0	0
ADD	0	1	0	0	0	0	0
MOV	0	1	0	0	0	0	0
NOT	0	1	0	0	0	0	0
INC	0	1	0	0	0	0	0
DEC	0	1	0	0	0	0	0
SUB	0	1	0	0	0	0	0
AND	0	1	0	0	0	0	0
OR	0	1	0	0	0	0	0

INST	А	.lu_O	P	Cin	M2R	SETC	/CLRC	RET,	/RTI	Call	OUT_signal
NOP	1	0	0	0	0	0	0	0	0	0	0
SETC	1	0	0	0	0	1	1	0	0	0	0
CLRC	1	0	0	0	0	1	0	0	0	0	0
CALL	1	0	0	0	0	0	0	0	0	1	0
JZ	1	0	0	0	0	0	0	0	0	0	0
JC	1	0	0	0	0	0	0	0	0	0	0
JMP	1	0	0	0	0	0	0	0	0	0	0
RET	1	0	0	0	0	0	0	1	0	0	0
RTI	1	0	0	0	0	0	0	1	1	0	0
POP	1	0	0	0	1	0	0	0	0	0	0
PUSH	1	0	0	0	0	0	0	0	0	0	0
IN	1	0	0	1	0	0	0	0	0	0	0
OUT	1	0	0	0	0	0	0	0	0	0	1
STD	1	0	0	0	0	0	0	0	0	0	0
IADD	0	0	0	0	0	0	0	0	0	0	0
LDM	1	0	0	1	0	0	0	0	0	0	0
LDD	1	0	0	0	1	0	0	0	0	0	0
ADD	0	0	0	0	0	0	0	0	0	0	0
MOV	1	0	0	0	0	0	0	0	0	0	0
NOT	1	0	1	0	0	0	0	0	0	0	0
INC	0	0	1	0	0	0	0	0	0	0	0
DEC	0	1	0	0	0	0	0	0	0	0	0
SUB	0	1	1	0	0	0	0	0	0	0	0
AND	1	1	0	0	0	0	0	0	0	0	0
OR	1	1	1	0	0	0	0	0	0	0	0

Schematic

 

Design Link: **DESIGN**

 

LOAD USE UNIT LOGIC:

```
LOAD <= '1'
WHEN ((Dec_Exec_MemRead='1'and((Dec_Exec_Rt=Fet_Dec_Rs)) or
(Dec_Exec_Rt=Fet_Dec_Rt)))
ELSE '1' WHEN
((Exec_Mem1_MemRead='1'and((Exec_Mem1_Rt=Fet_Dec_Rs)) or
(Exec_Mem1_Rt=Fet_Dec_Rt))))
-- ELSE '1' WHEN (Result='1')
Else '0';
```

CHANGES DONE TO DESIGN:

- Branching Logic moved from decode to execute stage to work with forwarding unit (placed also in execute Stage)
- Structural Hazard Detection unit moved from fetch to decode stage.
- Interrupt logic Changed.

Pipeline Registers Details

IF/ID REG (48 BITS):

INPUT	BITS	47-32	31-16	15-0	
	Signal	PC+1	INSTRUCTION	IMM/IN	

ID/IE REG (88 BITS):

Input	BITS	87-73	72-57	56-54	53-51	50-48	47-32	31-16	15-0
	SIGNAL	Controller	PC + 1	RSRC1	RSRC2	RDST	RSRC1	RSRC2	IMM OR
		Signals		ADD	ADD	ADD	Value	Value	IN

Controller Signals:

```
SET_CLEAR <= Decode_Buffer_OUT(87 downto 86);
Write_back <= Decode_Buffer_OUT(85);
MEM_SRC <= Decode_Buffer_OUT(84);
SP_INC <= Decode_Buffer_OUT(83);
SP_DEC <= Decode_Buffer_OUT(82);
MEM_WRITE <= Decode_Buffer_OUT(81);
Out_Signal <= Decode_Buffer_OUT(80);
ALU_SRC <= Decode_Buffer_OUT(79);
ALU_Operation <= Decode_Buffer_OUT(78 downto 76);
CIN_Signal <= Decode_Buffer_OUT(75);
CALL_Signal <= Decode_Buffer_OUT(74);
MEM_TO_REG <= Decode_Buffer_OUT(73);
```

IE/MEM1 REG (65 BITS):

Input	BITS	64-49	48-41	40-25	24-9	8-6	5-3	2-0
	SIGNAL	PC+1	Controller Signals	ALU_RESULT	RSRC2_VALUE	Rsrc1_add	Rsrc2_add	Rdst_add

Controller Signals:

```
Write_back <= EX_MEM1_Buffer(48);

MEM_SRC <= EX_MEM1_Buffer (47);

SP_INC <= EX_MEM1_Buffer (46);

SP_DEC <= EX_MEM1_Buffer (45);

MEM_WRITE <= EX_MEM1_Buffer (44);

Out_Signal <= EX_MEM1_Buffer (43);

CALL_Signal <= EX_MEM1_Buffer (42);

MEM_TO_REG <= EX_MEM1_Buffer (41);
```

Mem1/MEM2 REG (64 BITS):

Input	BITS	63-48	47-41	40-25	24-9	8-6	5-3	2-0
	SIGNAL	PC+1	Controller Signals	READ_ADD	WRITE_DATA	Rsrc1_add	Rsrc2_add	Rdst_add

Controller Signals:

```
WB_OUT <= BUFF_OUT(47);

MEM_TO_REG_OUT <= BUFF_OUT(46);

SP_INC_OUT <= BUFF_OUT(45);

SP_DEC_OUT <= BUFF_OUT(44);

MEMW_OUT <= BUFF_OUT(43);

OUT_SIG_OUT <= BUFF_OUT(42);

CALL_SIG_OUT <= BUFF_OUT(41);
```

MemSt2/Wb REG (44 BITS):

Input	BITS	43	42	41	40-25	24-9	8-6	5-3	2-0
	SIGNAL	Wb	M2r	outEn	Memst2	Memst1	RSRC1	RSRC2	Rdst
							Value	Value	